

Kirchoff's Laws:

Kirchoff's Loop Rule (Voltage Law)

The algebraic sum of the potential differences around any closed loop is zero.

Kirchoff's Junction Rule (Current Law)

The algebraic sum of all current into and out of a junction is zero.

(Currents entering: $I > 0$ Current leaving: $I < 0$)