

# Capacitance & Capactors

# What do the following all have in common?


- A compressed gas.      Internal Energy
- A stretched spring.      Elastic PE
- A raised mass.      Gravitational PE
- Glucose molecule.      Chemical PE

They all have (potential) energy stored in them.
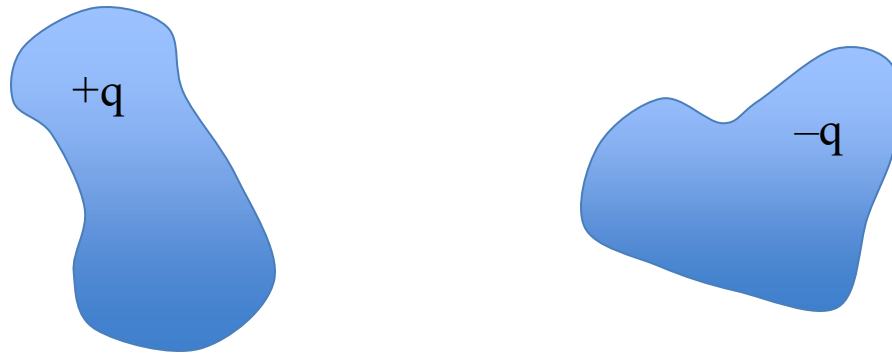
# Storing Electrical Potential Energy

A device that stores EPE is called a capacitor.

It consists of two isolated conductors with equal but opposite charges on them.



# Capacitance defined

Each conductor is an equipotential surface. Thus, there exists some potential difference between them. This  $\Delta V$  is found to be proportional to the magnitude of the charge on either conductor. That is,

$$|q| = C|\Delta V|$$

The proportionality constant,  $C$ , is defined as the “**capacitance**.”

$$C \equiv \left| \frac{\text{charge on either conductor}}{\text{potential difference between the conductors}} \right| = \left| \frac{q}{\Delta V} \right|$$



Note that  $C$  is ALWAYS a positive quantity.

# Capacitance

1.  $C$  describes how much (equal, but opposite) charge must be placed on the two conductors in order to produce a certain  $\Delta V$  between them.
2.  $C$  depends on NEITHER the charge  $q$  NOR the potential difference  $\Delta V$ , but rather only on the geometry of the conductors.
3.  $C$  has units of  $\left(\frac{\text{Coulombs}}{\text{Volt}}\right)$  defined as “Farads”

That is,  $1 \text{ F} \equiv 1 \text{ C/V}$ .

# Example 1: Parallel Plates

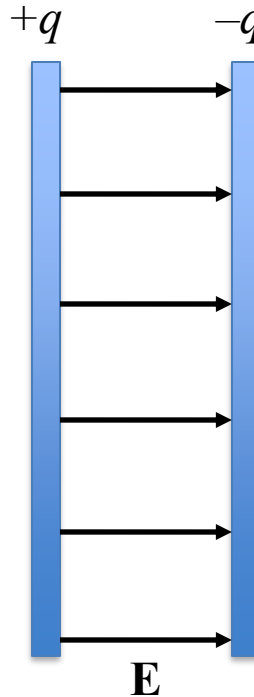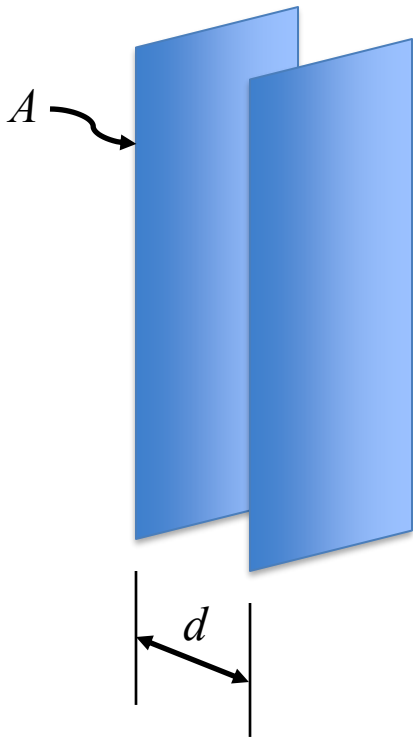

From Gauss law:


$$E = \frac{\sigma}{\epsilon_0} = \frac{q}{\epsilon_0 A}$$

Using  $\Delta V = - \int_A^B \vec{E} \cdot d\vec{s}$ :

$$\Delta V = -Ed = -\frac{q}{\epsilon_0 A} d$$

$$\text{So then, } C \equiv \left| \frac{q}{\Delta V} \right| = \frac{q}{\left( \frac{qd}{\epsilon_0 A} \right)} = \frac{\epsilon_0 A}{d}$$


## Example 2: Concentric Cylinders

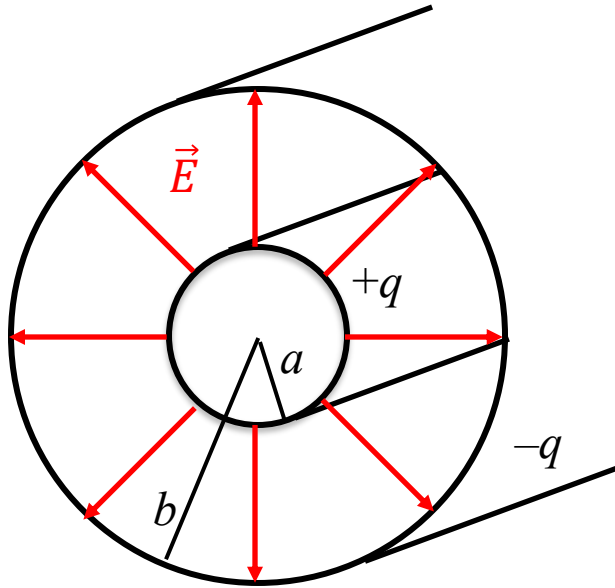

$$\begin{aligned}\Delta V &= - \int_a^b \vec{E} \cdot d\vec{s} \\ &= - \int_a^b E dr \\ &= - \int_a^b \frac{q}{2\pi\epsilon_0 L r} dr \\ &= - \frac{q}{2\pi\epsilon_0 L} \ln\left(\frac{b}{a}\right)\end{aligned}$$

$$\therefore C \equiv \left| \frac{q}{\Delta V} \right| = \frac{2\pi\epsilon_0 L}{\ln\left(\frac{b}{a}\right)}$$

# Example 3: Concentric Spheres

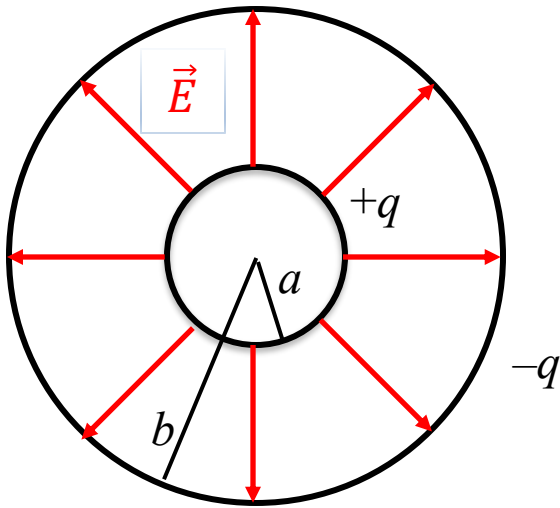

$$\begin{aligned}\Delta V &= - \int_a^b \vec{E} \cdot d\vec{s} \\ &= - \int_a^b E dr \\ &= - \int_a^b \frac{q}{4\pi\epsilon_0 r^2} dr \\ &= \frac{q}{4\pi\epsilon_0} \left( \frac{1}{b} - \frac{1}{a} \right)\end{aligned}$$

$$\therefore C \equiv \left| \frac{q}{\Delta V} \right| = \frac{4\pi\epsilon_0}{\left( \frac{1}{b} - \frac{1}{a} \right)} = \frac{4\pi\epsilon_0 ab}{(b - a)}$$



# Questions...

What is the capacitance of an isolated conducting sphere?

Answer: This is just the previous example while letting  $b \rightarrow \infty$ . That is...


$$C = \frac{4\pi\epsilon_0}{\left(\frac{1}{\cancel{b}} - \frac{1}{a}\right)} \rightarrow 4\pi\epsilon_0 a$$

0

Calculate the capacitance of a conducting sphere that is the size of the Earth ( $R_{Earth} = 6370$  km).

$$C = 708 \mu\text{F}$$

# Parallel Combinations

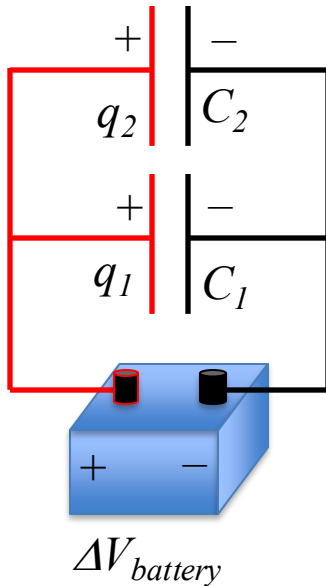


The battery transfers electrons from the left plates to the right plates. Note that each capacitor has the same  $\Delta V_{battery}$  across them.

The total charge separated on the capacitors is  $q = q_1 + q_2$ .

$$C_{equiv} = \frac{q}{\Delta V} = \frac{q_1 + q_2}{\Delta V} = \frac{q_1}{\Delta V} + \frac{q_2}{\Delta V} = C_1 + C_2$$

Extending to  $N$  capacitors:  $C_{equiv} = \sum_{i=1}^N C_i$

# Series Combinations

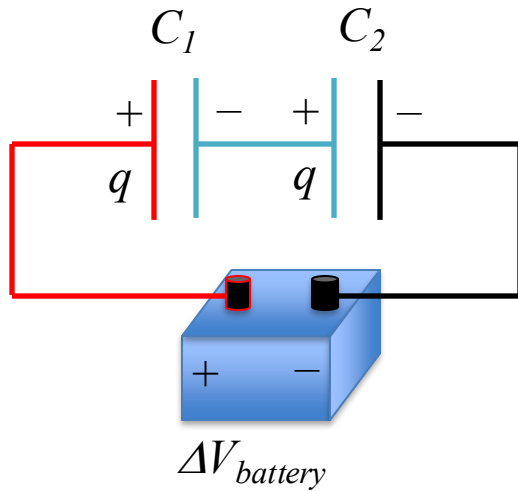

The battery transfers electrons from the left plate of  $C_1$  and the right plate of  $C_2$ .

No charge is transferred to the inner plates.


Note that each capacitor has the same charge  $q$  on each plate  $\Delta v_{battery}$ .

$$\Delta V_{battery} = \frac{q}{C_{equiv}} \text{ across the combination is } \Delta V_1 + \Delta V_2 = \frac{q}{C_1} + \frac{q}{C_2}$$

$$\text{Then } \frac{1}{C_{equiv}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\text{For } N \text{ capacitors: } \frac{1}{C_{equiv}} = \sum_{i=1}^N \frac{1}{C_i}$$

# Example #1

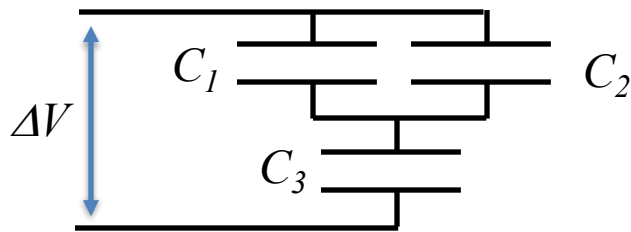

$$C_1 = 12.0 \mu\text{F}$$

$$C_2 = 5.30 \mu\text{F}$$

$$C_3 = 4.50 \mu\text{F}$$

$$\Delta V = 12.5 \text{ V}$$

Determine  $C_{equiv}$

$C_1$  and  $C_2$  are in parallel:



$$C_{12} = C_1 + C_2 = 12.0 \mu\text{F} + 5.30 \mu\text{F} = 17.3 \mu\text{F}.$$

$C_{12}$  and  $C_3$  are in series:


$$\frac{1}{C_{equiv}} = \frac{1}{C_{12}} + \frac{1}{C_3} = \frac{1}{17.3 \mu\text{F}} + \frac{1}{4.50 \mu\text{F}} = 0.280 \mu\text{F}^{-1}$$

$$C_{equiv} = 3.57 \mu\text{F}$$

Solution:

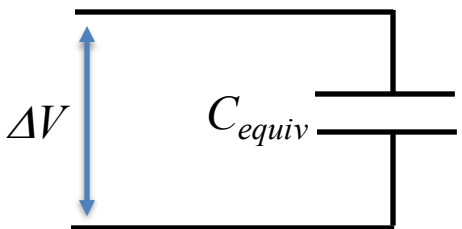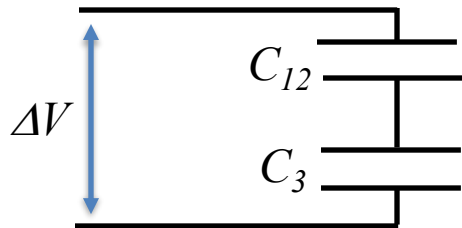

# Example #1 cont'd

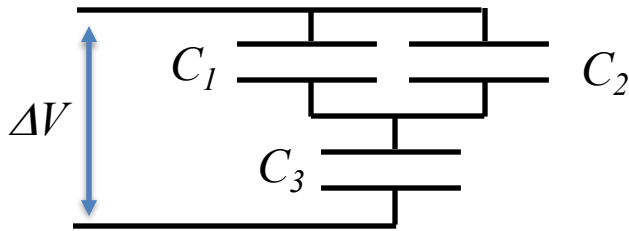

$$C_1 = 12.0 \mu\text{F}$$

$$C_2 = 5.30 \mu\text{F}$$

$$C_3 = 4.50 \mu\text{F}$$

$$\Delta V = 12.5 \text{ V}$$

Determine the  $q_1$  on  $C_1$ .


Solution: Knowing  $C_{equiv}$  has same  $\Delta V$  as the battery, the total charge on the network is  $q_{total} = C_{equiv} \Delta V = (3.57 \mu\text{F})(12.5 \text{ V}) = 44.6 \mu\text{F}$ .

Working backwards, this is the charge on  $C_3$  and  $C_{12}$  since they are in series. The  $\Delta V$  across  $C_1$  and  $C_2$  is the same as  $C_{12}$  since  $C_1$  and  $C_2$  are in parallel.  $\Delta V_{12} = C_{12}/q_{total} = 17.3 \mu\text{F} / 44.6 \mu\text{F} = 2.58 \text{ V}$ .

$$\text{So, } q_1 = C_1 \Delta V_1 = (12.0 \mu\text{F})(2.58 \text{ V})$$

$$q_1 = 31.0 \mu\text{C}$$

# Example #2

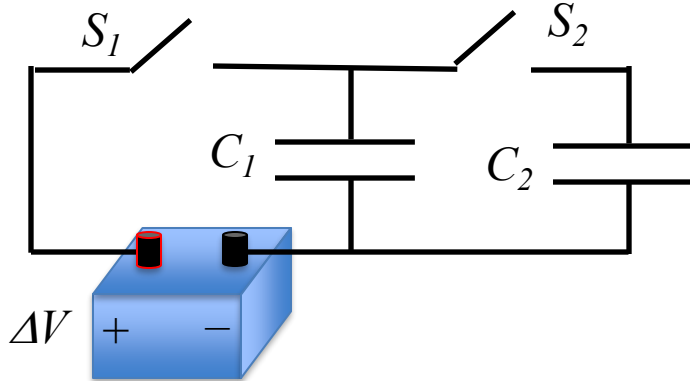

$$C_1 = 3.55 \mu\text{F} \quad C_2 = 8.95 \mu\text{F}$$

$$\Delta V = 6.30 \text{ V}$$

Close  $S_1$  to fully charge  $C_1$ .


Open  $S_1$ , then close  $S_2$ .

Wait until  $\Delta V_1 = \Delta V_2 = \Delta V_f$ .

Determine  $\Delta V_f$ .

$$\Delta V_f = 1.79 \text{ V}$$

# Solution to Example #2

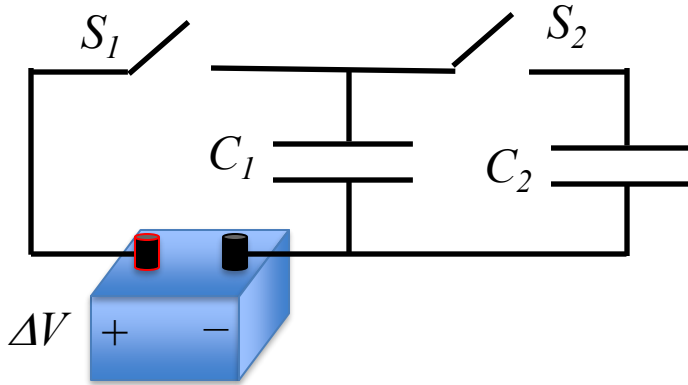

When  $S_1$  is closed,  $C_1$  acquires a charge  $q_{1i} = C_1 \Delta V$ .

When  $S_1$  is opened, the charge remains on  $C_1$ .

When  $S_2$  is closed, some of the  $q_{1i}$  transfer to  $C_2$  until

$$\Delta V_1 = \Delta V_2 = \Delta V_f.$$

Conservation of charge required that  $q_{1f} + q_{2f} = q_{1i}$ .

$$C_1 \Delta V_f + C_2 \Delta V_f = C_1 \Delta V$$

$$\text{Solve for } \Delta V_f = \frac{C_1 \Delta V}{C_1 + C_2} = \frac{(3.55 \mu F)(6.30 \text{ V})}{3.55 \mu F + 8.95 \mu F} = 1.79 \text{ V}$$

# Energy Stored in the **E**-field

In order to move charge from one conductor to the other, you need to do WORK.

If  $q$  already on plates, giving a potential difference  $\Delta V$  at that instant,

$$\Delta V = -\frac{W_{field}}{q} = \frac{W_{ext}}{q}$$

$$dW_{ext} = \Delta V dq = \frac{q}{C} dq$$

$$W_{ext} = \int dW_{ext} = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C} = \Delta U_E$$




# Dielectrics


Dielectric: An insulating material placed between the oppositely charged conductors that alters the capacitance as it becomes polarized upon insertion.

The new capacitance,  $C' = \kappa C$ ,  
where  $\kappa \equiv$  dielectric constant.

$\kappa \geq 1$ . ( $\kappa_{\text{vacuum}} = 1$ )
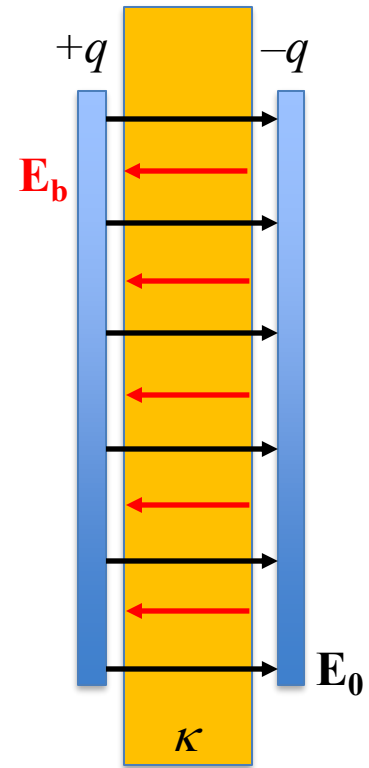
$$E_{\text{total}} = E_0 - E_b = \frac{E_0}{\kappa}, \text{ since } E_{\text{total}} = \frac{\Delta V_{\text{new}}}{d} = \frac{\frac{\Delta V}{\kappa}}{d} = \frac{E_0}{\kappa}$$



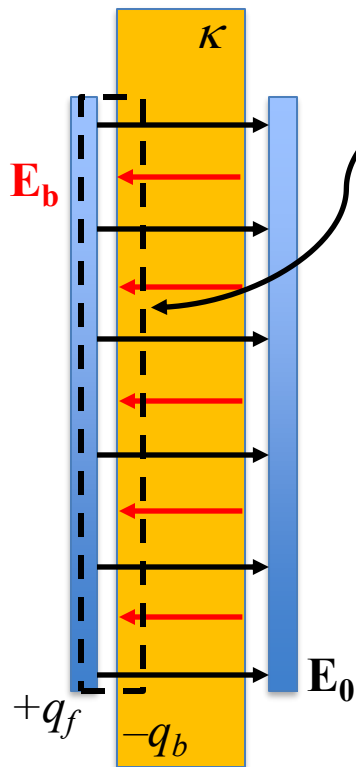

Gaussian “box”

$$\oint \vec{E} \cdot d\vec{A} = E_{total}A = (E_0 - E_b)A$$

$$E_{total} = \frac{q_{enc}}{\epsilon_0 A} = \frac{q_f - q_b}{\epsilon_0 A}$$

$$E_{total} = \frac{\sigma_f - \sigma_b}{\epsilon_0}$$

$$\therefore E_b = E_0 - \frac{E_0}{\kappa} = E_0 \left(1 - \frac{1}{\kappa}\right).$$


Recall that  $1 < \kappa < \infty$ . So,  $E_b$  is always less than  $E_0$ .

Also, since  $E \propto \sigma$ ,  $\sigma_b = \sigma_f \left(1 - \frac{1}{\kappa}\right)$   $\sigma_b$  is always less than  $\sigma_f$ .



For  $\kappa = 1$ :  $\sigma_b = 0$  (No dielectric inserted.)

For  $\kappa = \infty$ :  $\sigma_b = \sigma_f$  (Conducting slab inserted.)


# Composite Capacitors

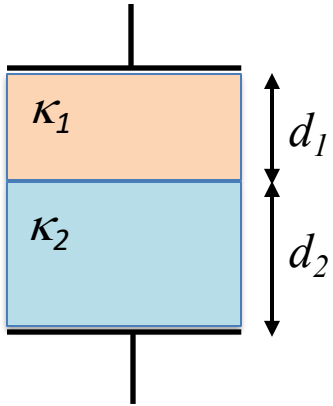

Treat as capacitors  
in series:

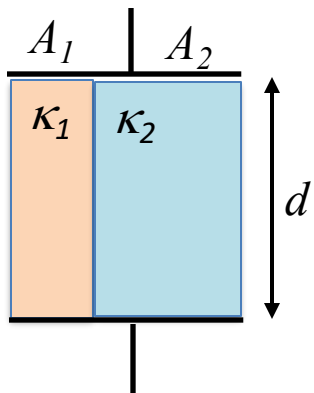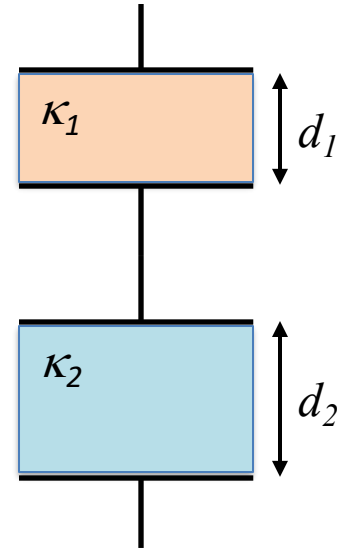

Treat as capacitors  
in parallel.

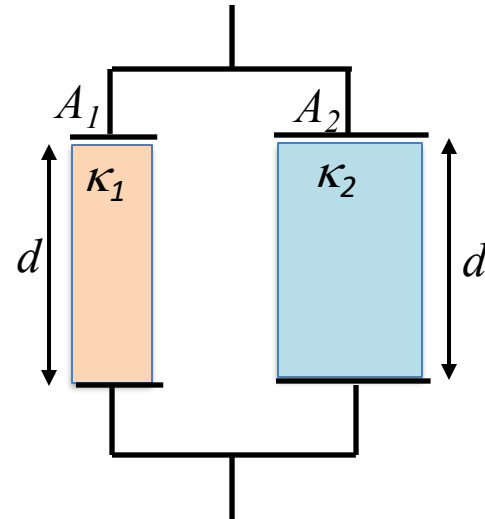


# Two cases:

1) Inserting the dielectric with the battery attached:

$$\Delta V = \text{constant}$$

$$C' = \kappa C$$

$$q' = \kappa q$$

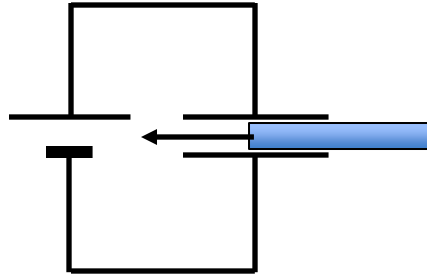

2) Inserting the dielectric with the battery disconnected:

$$q = \text{constant}$$

$$C' = \kappa C$$

$$\Delta V' = \Delta V / \kappa$$

