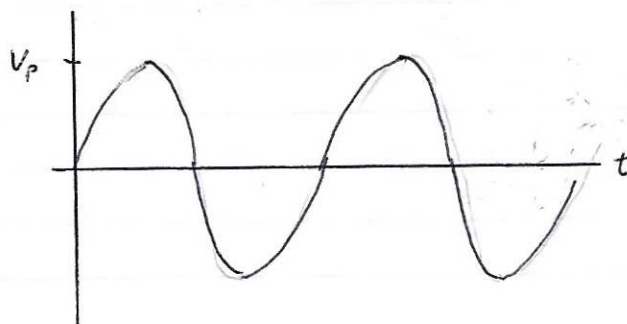


AC Circuits



We'll see why this is a useful quantity later.

$$V_{rms} = \frac{V_p}{\sqrt{2}}$$

root mean square

$$= \left[\text{average of } V_p^2(t) \right]^{1/2} = \sqrt{V_p^2}$$

$$= \left[\frac{1}{T} \int_0^T V_p^2 \sin^2 \omega t dt \right]^{1/2}$$

$$\omega = \text{ang. freq.} = 2\pi f$$

In general, $V(t) = V_p \sin(\omega t + \phi_v)$


other texts use E_p, E_{max}, V_{max} for V_p .

Similarly, $I(t) = I_p \sin(\omega t + \phi_i)$

traditionally written with '-' sign

Resistive Load

(Let $\phi_v = 0$)

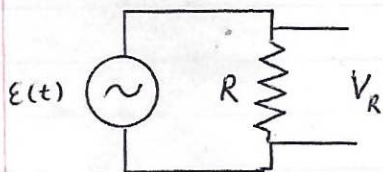

$$E(t) = E_{max} \sin \omega_d t \quad I = I_{max} \sin(\omega t - \phi)$$


$$E - V_R = 0$$

$$\phi = \phi_v - \phi_i$$


$$\therefore V_R = E = E_{max} \sin \omega_d t$$

So $V_R = V_{Rmax} \sin \omega_d t$ and $I_R = \frac{V_R}{R} = \frac{V_{Rmax}}{R} \sin \omega_d t$
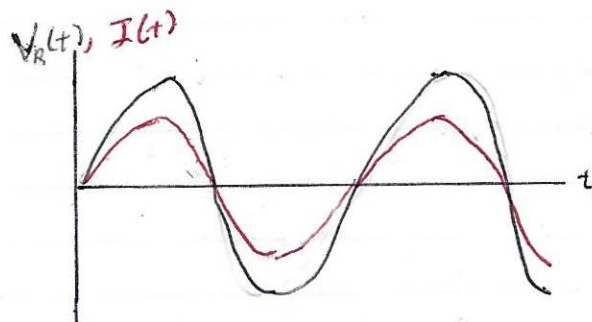
$$V_R = I_R R \text{ (resistor)} \quad \boxed{\phi = 0^\circ} \quad \text{Current is in phase with } V_R.$$



Inductive Load

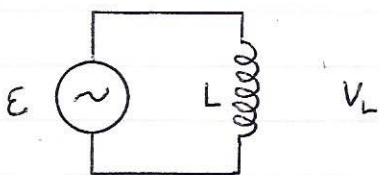

$$V_L = V_{L \max} \sin \omega_d t \quad \text{Let } \phi_v = 0$$

$$\uparrow = L \frac{dI}{dt}$$

$$\frac{dI}{dt} = \frac{V_{L \max}}{L}$$

$$I_L = \int dI = \frac{V_{L \max}}{L} \int \sin \omega_d t \, dt = -\frac{V_{L \max}}{L \omega_d} \cos \omega_d t$$

$$= -\frac{V_{L \max}}{X_L} \cos \omega_d t$$

where $X_L = \omega_d L = \text{inductive reactance}$
Units of " Ω "

$$= \frac{V_L}{X_L} \sin(\omega_d t - 90^\circ)$$

Again: $\phi = \phi_v - \phi_i = -\phi_i$


$$I = I_{\max} \sin(\omega_d t + \phi_i)$$

$$= \dots (-\phi)$$

$$I_L = I_{\max} \sin \omega_d t - 90^\circ$$

$\phi = +90^\circ$ for pure inductive load

$$V_L = I_L X_L$$

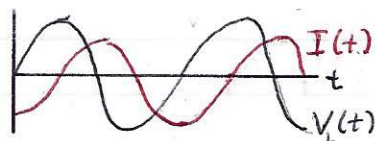

I_L lags V_L (or V leads I) since changing current induces a "back EMF"


Before I can build up significantly, there must first be a V across the inductor.

$X_L = \omega L$ As $f \rightarrow 0$, $X_L \rightarrow 0$. Since rate of change of current $\rightarrow 0$

'L' behaves like a SHORT CIRCUIT

As $f \rightarrow \infty$, $X_L \rightarrow \infty$. The faster I changes, the more vigorously the L opposes that change.
'L' behaves like an OPEN CIRCUIT

Capacitive Load

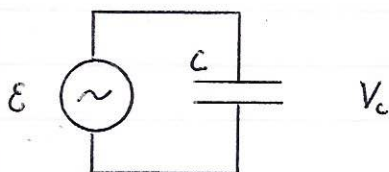

$$V_c = V_{c_{max}} \sin \omega_d t \quad \text{Let } \phi_v = 0^\circ$$

$$q_c = CV_c = CV_{c_{max}} \sin \omega_d t$$

$$I_c = \frac{dq}{dt} = \omega_d CV_{c_{max}} \cos \omega_d t$$

$$= \omega_d CV_{c_{max}} \sin(\omega_d t + 90^\circ)$$

$$I_c = \frac{V_c}{X_c} \sin(\omega_d t + 90^\circ) \quad \text{where } X_c = \frac{1}{\omega_d C} = \text{capacitive reactance}$$

Note: $I = I_{max} \sin(\omega_d t + \phi_i)$

$$\therefore \phi = \phi_v - \phi_i = -90^\circ \quad (\text{Let } \phi_v = 0)$$


$$I = I_{max} \sin(\omega_d t - \phi)$$

$$X_c = \frac{1}{\omega_d C}, \quad \omega = 2\pi f$$

$$\text{As } f \rightarrow 0, \quad X_c \rightarrow \infty$$

$$\text{As } f \rightarrow \infty, \quad X_c \rightarrow 0$$

for pure capacitive load

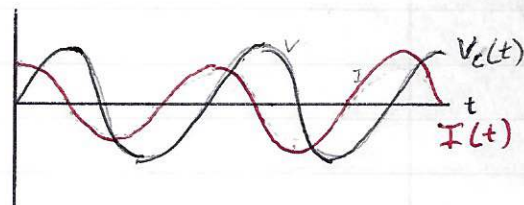


$f = 0 \Rightarrow$ No change in V_c
 $\therefore$ No charge on or off.
C behaves like an OPEN CIRCUIT

Current moves charge on & off in increasingly shorter times.
 $\therefore$ **C behaves like a SHORT CIRCUIT**

I leads V since $V_c \propto q$ and it takes current to move the charge

$\therefore$ **I flows before V** changes significantly.

Series RLC Circuit

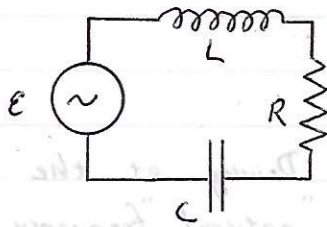

$$\mathcal{E}(t) = \mathcal{E}_{\max} \sin \omega_d t$$

If all elements in series;
all have same current



$$I_L = I_R = I_C = I = I_{\max} \sin(\omega_d t - \phi)$$

(Again, let $\phi_v = 0$)


Kirchoff:

$$\mathcal{E} = V_L + V_R + V_C = \mathcal{E}_{\max} \sin \omega_d t$$

Phasors

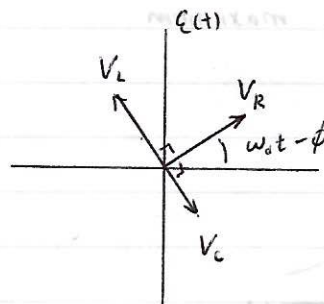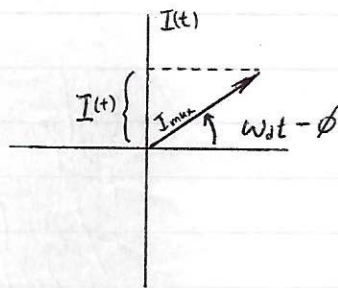

Vector sum

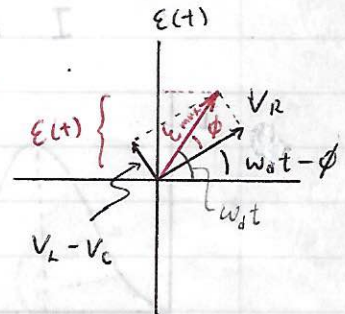

$$\mathcal{E}^2 = V_R^2 + (V_L - V_C)^2 = (IR)^2 + [(IX_L) - (IX_C)]^2$$

$$I = \frac{\mathcal{E}}{[R^2 + (X_L - X_C)^2]^{1/2}} = \frac{\mathcal{E}}{Z}$$

Define impedance, $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$$= \sqrt{R^2 + (\omega_d L - \frac{1}{\omega_d C})^2}$$

$$\text{Also, } \tan \phi = \frac{V_L - V_C}{V_R} = \frac{IX_L - IX_C}{IR} = \frac{X_L - X_C}{R}$$

If $X_L > X_C$ $\phi > 0$ $I_{\max}$ rotates behind $\mathcal{E}_{\max}$: inductive circuit

$X_L < X_C$ $\phi < 0$ $I_{\max}$ " ahead of $\mathcal{E}_{\max}$: capacitive circuit

$X_L = X_C$ $\phi = 0$ $I_{\max}$ & $\mathcal{E}_{\max}$ rotate together in phase : resonance

Resonance

$$X_L = X_C, \phi = 0$$

$$\omega L = \frac{1}{\omega C} \rightarrow \omega = \frac{1}{\sqrt{LC}}$$






Driving at the "natural frequency" of the circuit

Use "L is in the left and C is in the collar."

At resonance : $Z = Z_{\min}$ since $Z = [R^2 + (X_L - X_C)^2]^{\frac{1}{2}}$

I is a maximum

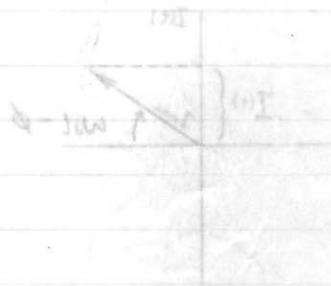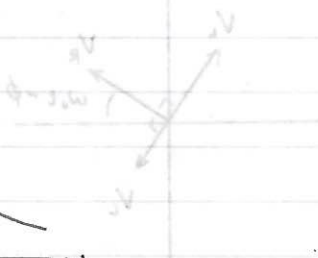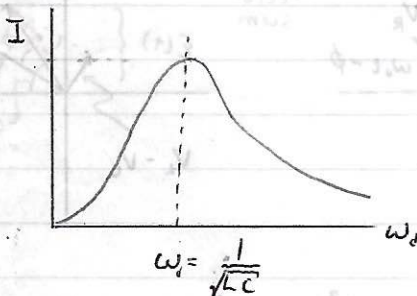

Phasors

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

Define impedance $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{IX_L - IX_C}{IR} = \frac{X_L - X_C}{R}$$

If $X_L > X_C$ $\phi > 0$ I lags V (inductive circuit)

If $X_L < X_C$ $\phi < 0$ I leads V (capacitive circuit)

If $X_L = X_C$ $\phi = 0$ I and V are in phase (resonance)